

R_1	$=$	$50\,\Omega$	R_2	$=$	$1\,\text{k}\Omega$	R_3	$=$	$0,5\,\text{k}\Omega$	R_4	$=$	$1\,\text{k}\Omega$
R_5	$=$	$1,5\,\text{k}\Omega$	R_6	$=$	$2\,\text{k}\Omega$	R_7	$=$	$1,5\,\text{k}\Omega$	R_8	$=$	$2\,\text{k}\Omega$
R_9	$=$	$2,5\,\text{k}\Omega$	R_{10}	$=$	$3\,\text{k}\Omega$	R_{11}	$=$	$2,5\,\text{k}\Omega$	I_{q1}	$=$	$2\,\text{mA}$
U_{q1}	$=$	$1,5\,\text{V}$	U_{q2}	$=$	$3\,\text{V}$	U_{q3}	$=$	$4,5\,\text{V}$	I_{q2}	$=$	$4\,\text{mA}$